
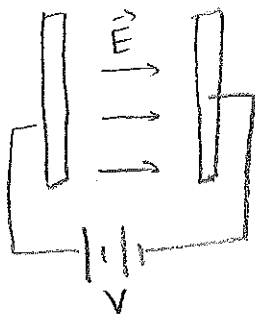


Electrical conductors

An electron placed in vacuum between parallel plates will accelerate γ

$$\vec{a} \propto \vec{E}$$
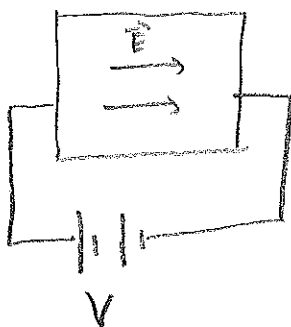
$$(\vec{a} = \frac{\vec{F}}{m} = -\frac{e\vec{E}}{m})$$



A conductor is a solid material (e.g. metal) γ a certain density n of conduction electrons

- fixed lattice of positive nuclei
- tightly bound core electrons
- "see" of conduction electrons that move relatively freely through the conductor (maintaining local neutrality, i.e. others move in to take their place)
- each atom contributes 1 or more conduction e^- s

e.g. copper: $n = 8.5 \times 10^{28} \frac{e^-}{m^3}$ [$\approx \frac{\# \text{ atoms}}{m^3}$]


In the electric field created by a battery the conduction electrons move γ constant drift velocity

$$\vec{v}_d \propto \vec{E}$$

- due to collisions γ impurities, accelerating electrons soon reach a terminal velocity, like objects falling γ a drag force

$v_d \sim \text{few } \frac{\text{cm}}{\text{hr}}$; actual random velocities much higher but avg to zero if $\vec{E} = 0$

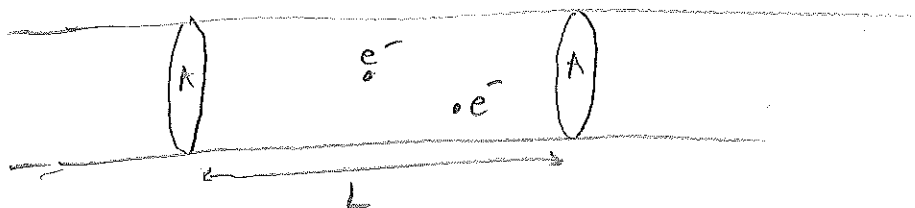Consider a conductor in the shape of a cylinder
 w/ cross-section A



How much charge due to conduction electrons in length L ?

$$\Delta q = (\text{charge per electron}) \left(\frac{\# \text{ conduction electrons}}{\text{volume}} \right) (\text{volume})$$

$$= (-e)(n)(AL)$$

If conduction electrons move w/ speed v_d , how long Δt until all of them pass through a plane bisecting the conductor?

$$v_d \Delta t = L \quad \Rightarrow \quad \Delta t = \frac{L}{v_d}$$

What is the current through the plane?

$$i = \frac{\Delta q}{\Delta t} = \frac{-neAL}{\left(\frac{L}{v_d}\right)} = -neAv_d$$

Define current density $\vec{j} = \frac{\text{current}}{\text{cross-sectional area}} = \frac{i}{A} = -nev_d$

Current density is a vector pointing in direction of current flow

$$\vec{j} = -ne\vec{v}_d$$

$\vec{j}$ opposite $\vec{v}_d$
 because electrons
 are negatively charged.

We learned that $\vec{v}_d \propto -e\vec{E}$

$$\Rightarrow \vec{j} \propto \vec{E}$$

Define conductivity σ as the constant of proportionality


$$\vec{j} = \sigma \vec{E}$$

σ depends on the material of the conductor

Also define

$$\text{Resistivity } \rho = \frac{1}{\sigma}$$

$$\Rightarrow \vec{E} = \rho \vec{j}$$

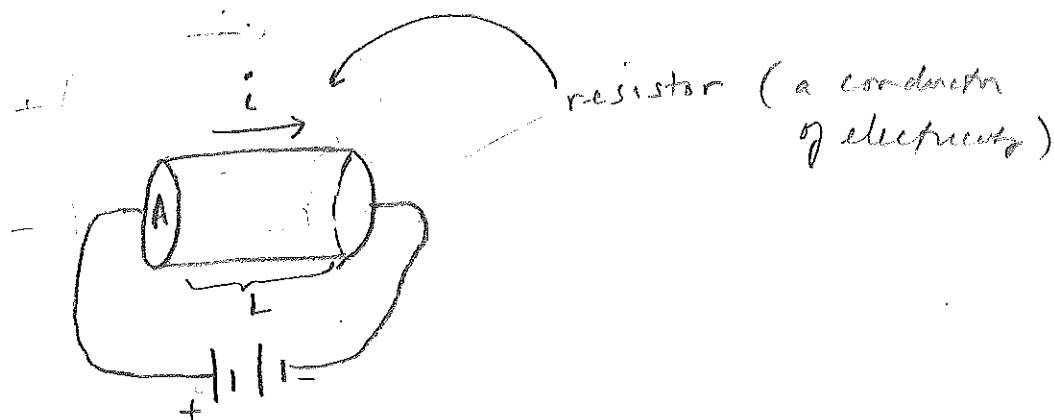

$i = \text{constant at all points along circuit (steady state)}$
 due to charge conservation (no charge buildup)

If resistor has constant cross-section A ,

then $j = \text{constant throughout} = \frac{i}{A}$

Since $\vec{E} = \rho \vec{j}$, $\vec{E}$ is also uniform through resistor

$$\Rightarrow \text{Voltage difference } \Delta V = - \int \vec{E} \cdot d\vec{r}$$


$$= EL$$

$$= \rho j L$$


$$= \frac{\rho i}{A} L$$

$$\Rightarrow \text{voltage across the resistor } V = i \left(\frac{\rho L}{A} \right)$$

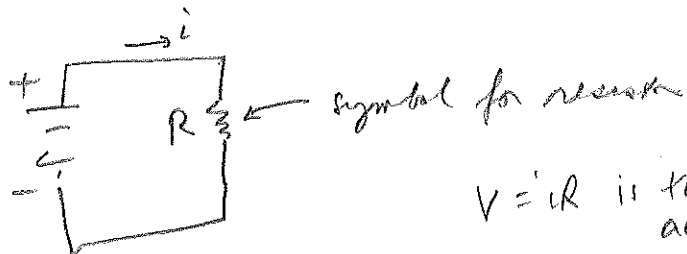Ohm's law: $V = iR$ where resistance $R = \frac{\rho L}{A}$



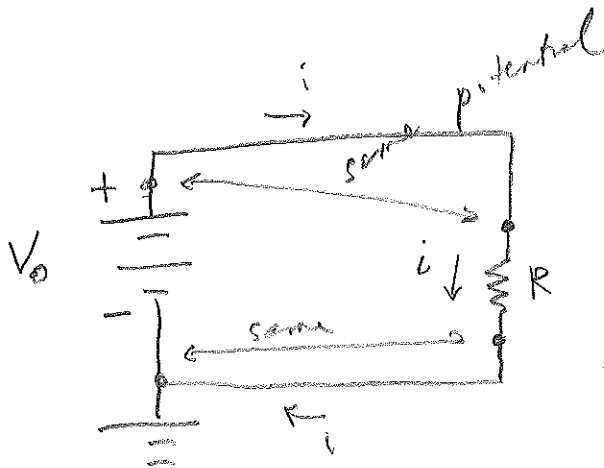$V = iR$ is the "voltage drop" across a resistor




The potential difference or "voltage drop" across a resistor

$$\Delta V = iR$$

$$V_0 = \Delta V \Rightarrow i = \frac{V_0}{R}$$

[the wires in a circuit are conductors w/ very low resistance ($\rho \approx 0$) so voltage drop (for given i) is very small.]

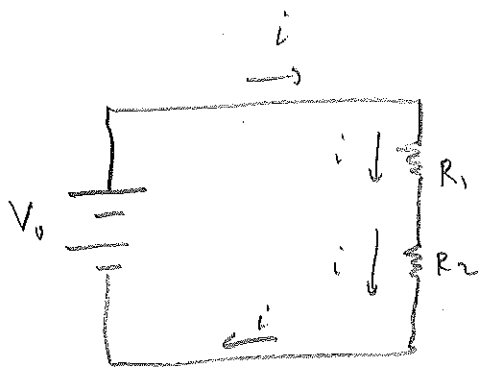Thus voltage at top of R is same as voltage at positive terminal of battery & the voltage at bottom is $\approx$ neg. terminal of battery]



$$\Delta V_1 = iR_1$$


$$\Delta V_2 = iR_2$$

$$V_0 = \Delta V_1 + \Delta V_2$$

$$= iR_1 + iR_2$$


$$= i(R_1 + R_2)$$

$$i = \frac{V_0}{R_1 + R_2}$$

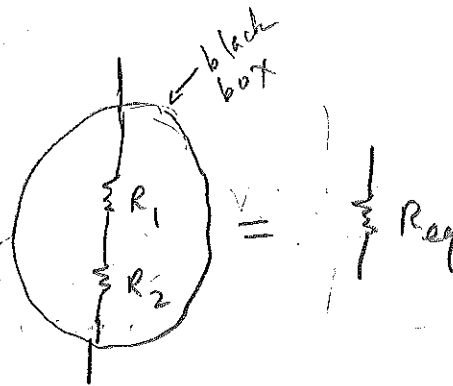


Two resistors connected in series are equivalent to a single resistor w/ resistance

$$R_{eq} = R_1 + R_2$$

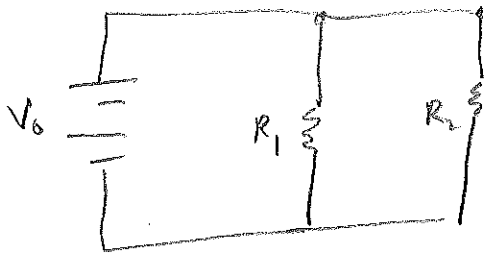

Voltage drop across each resistor connected in parallel is the same


$$\Delta V_1 = \Delta V_2 = V_0$$

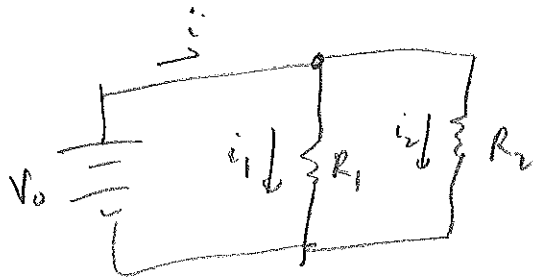

Kirchoff's current law $\Rightarrow i = i_1 + i_2$

$$\text{ohm} \Rightarrow i_1 = \frac{V_0}{R_1}, i_2 = \frac{V_0}{R_2}$$
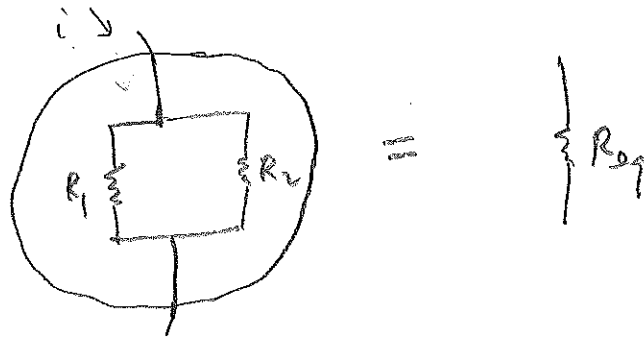
$$i = \left(\frac{1}{R_1} + \frac{1}{R_2} \right) V_0 = \frac{1}{R_{eq}} V_0$$



Two resistors connected in parallel are equivalent to a single resistor R_{eq} where

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$