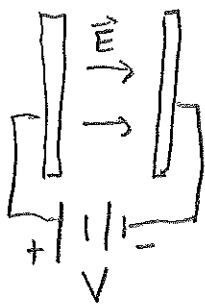


Electrical conductors

[Let's put these abstract concepts to use]




In vacuum, an electric field $\vec{E}$
acting on an electron results in acceleration

$$\vec{a} \propto -e\vec{E}$$

$$\text{because } \vec{a} = \frac{\vec{F}}{m} = \frac{q\vec{E}}{m}$$

[see "Electron gun" problem]

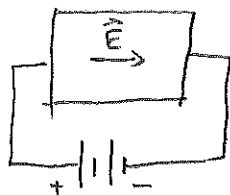

In a conductor, an electric field $\vec{E}$
acting on conduction electrons results in
constant drift velocity

$$\vec{v}_d \propto -e\vec{E}$$

[Discuss conductor: solid material w/
fixed lattice of positive nuclei,
tightly bound core electrons
+ "sea" of conduction electrons]

e.g. copper: 1 conduction electron per atom

$$n_c = \text{conduction electron number density} = 8.5 \times 10^{28} \frac{\text{electrons}}{\text{m}^3}$$

[Conduction electrons move in response to electric field
maintaining local neutrality, 7 others moving in to replace them]

[Collisions w/ impurities (similar to drag force)
cause accelerating electrons to reach a
terminal, or drift, velocity.
(Random velocities are much higher).]


Key takeaways:

1) $\vec{j} = \frac{1}{\rho} \vec{E}$ where $\vec{j}$ = current density
 ρ = resistivity of material

2) $V = iR$ (Ohm's law) where R = resistance

3) For a cylindrical resistor of length L and area A ,

$$R = \frac{\rho L}{A}$$

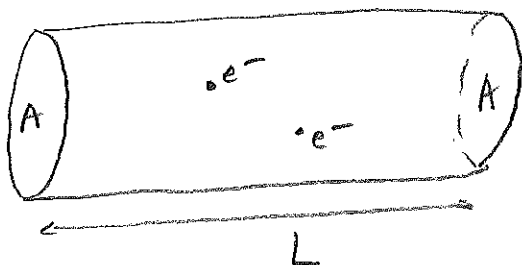

How much charge due to conduction electrons in resistor?

$$\Delta q = (\text{charge per electron}) \left(\frac{\# \text{ conduction electrons}}{\text{volume}} \right) (\text{volume})$$

$$= (-e) n_c (AL)$$

If conduction electrons move w/ constant speed v_d
how long Δt until all pass through a plane
bisecting the conductor?

$$v_d \Delta t = L \quad \Rightarrow \quad \Delta t = \frac{L}{v_d}$$

What is the current through the plane?

$$i = \frac{\Delta q}{\Delta t} = \frac{-n_e A L}{\left(\frac{L}{v_d}\right)} = -n_e A v_d$$

Define current density $\vec{j} = \frac{\text{current}}{\text{cross-sectional area}} = \frac{i}{A} = -n_e v_d$

Current density is a vector pointing in direction of current flow

$$\vec{j} = -n_e \vec{v}_d$$

[Why is $\vec{j}$ opposite $\vec{v}_d$?

Because charge carriers
are negative]

Earlier, we learned the $\vec{v}_d \propto -e\vec{E}$

therefore $\vec{j} \propto ne^2\vec{E}$ [$\vec{j}$ same direction as $\vec{E}$]

Call the constant of proportionality between $\vec{j}$ and $\vec{E}$


$\sigma \equiv$ conductivity of the material

$$\vec{j} = \sigma \vec{E}$$


Alternatively, define resistivity $\rho \equiv \frac{1}{\sigma}$

$$\boxed{\vec{j} = \frac{\vec{E}}{\rho}}$$

$$\Rightarrow \vec{E} = \rho \vec{j}$$

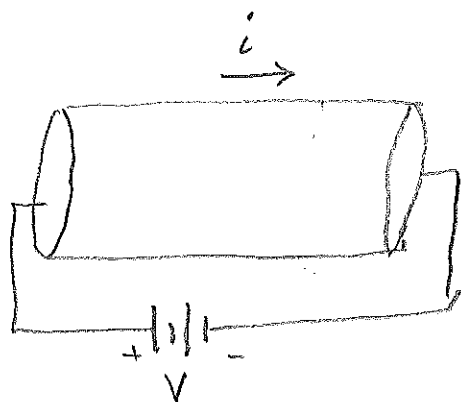

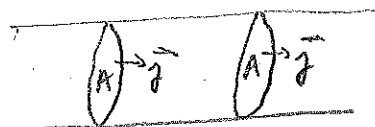- In steady-state conduction, current is same at all points in circuit (If not, charge will build up at certain points $\Rightarrow$ not steady state)



- If resistor has constant cross-section, then $\vec{j} = \text{constant}$

- since $\vec{E} = \rho \vec{j} \Rightarrow \vec{E}$ is uniform through resistor

- Voltage difference across resistor

$$\Delta V = V_+ - V_- = - \int_-^+ \vec{E} \cdot d\vec{r} = EL$$


Therefore

$$\Delta V = EL = \rho j L = \rho \frac{V}{A} L = \left(\frac{\rho L}{A} \right) i$$


"Voltage drop" across resistor is proportional to current (Ohm's law)

$$\boxed{V = iR}$$

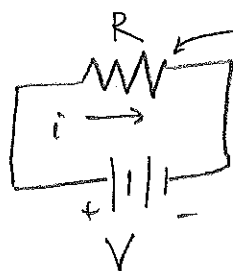where for cylindrical resistors $\boxed{R = \frac{\rho L}{A}}$



symbol for resistor

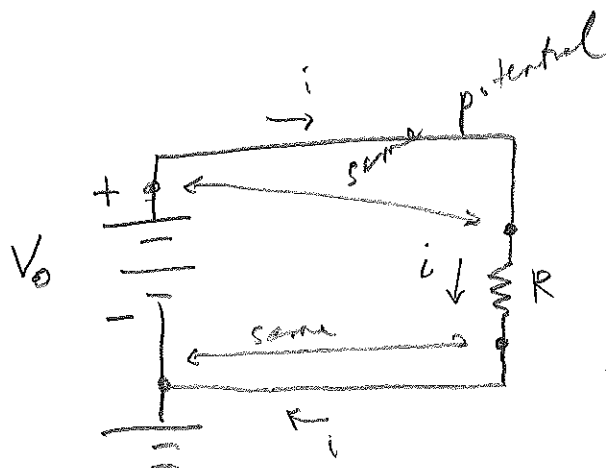


The potential difference or "voltage drop" across a resistor

$$\Delta V = iR$$

$$V_0 = \Delta V \Rightarrow i = \frac{V_0}{R}$$

[the wires in a circuit are conductors w/ very low resistance ($\rho \approx 0$) so voltage drop (for given i) is very small.]

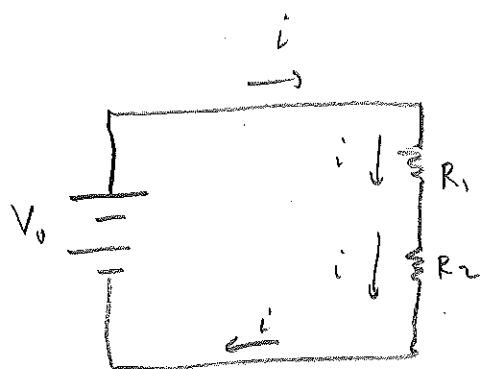Thus voltage at top of R is same as voltage at positive terminal of battery & the voltage at bottom is $\approx$ neg. terminal of battery]



$$\Delta V_1 = iR_1$$


$$\Delta V_2 = iR_2$$

$$V_0 = \Delta V_1 + \Delta V_2$$

$$= iR_1 + iR_2$$


$$= i(R_1 + R_2)$$

$$i = \frac{V_0}{R_1 + R_2}$$

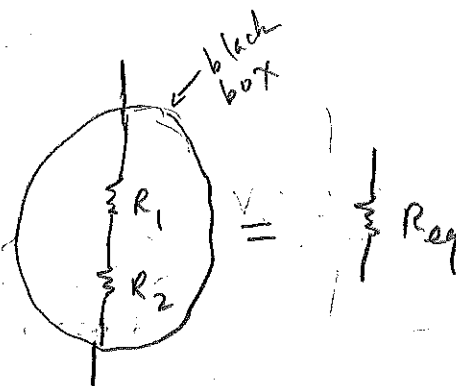


Two resistors connected in series are equivalent to a single resistor w/ resistance

$$R_{eq} = R_1 + R_2$$

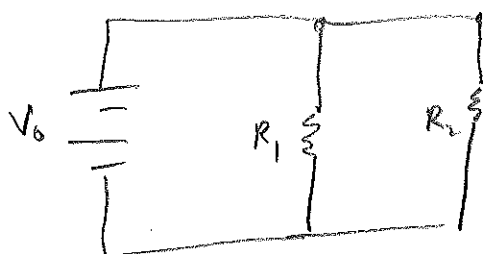

Voltage drop across each resistor connected in parallel is the same


$$\Delta V_1 = \Delta V_2 = V_0$$

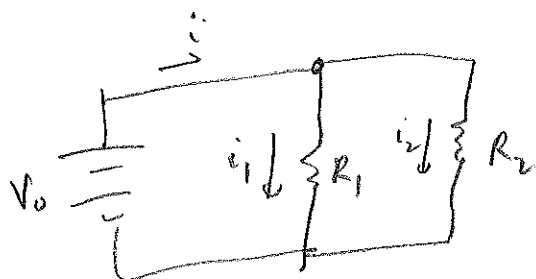

Kirchoff's current law $\Rightarrow i = i_1 + i_2$

$$\text{ohm} \Rightarrow i_1 = \frac{V_0}{R_1}, i_2 = \frac{V_0}{R_2}$$
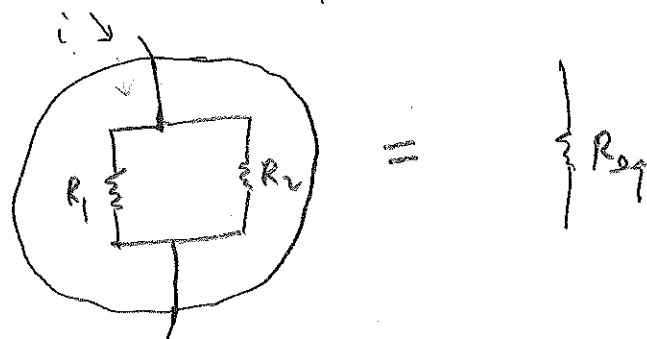
$$i = \left(\frac{1}{R_1} + \frac{1}{R_2} \right) V_0 = \frac{1}{R_{eq}} V_0$$



Two resistors connected in parallel are equivalent to a single resistor R_{eq} where

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$