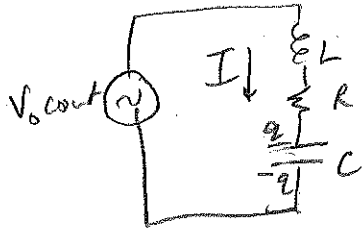


mechanical damped driven oscillator $m\ddot{x} + b\dot{x} + kx = F_0 \cos \omega t$

[They've seen RLC circuits in the problem set]

RLC circuit w/ AC driving voltage



Let q = charge on capacitor (upper plate)

$$I = \frac{dq}{dt}$$

$$V_L + V_R + V_C = V_0 \cos \omega t$$

$$L \frac{dI}{dt} + RI + \frac{q}{C} = V_0 \cos \omega t$$

$$L \ddot{q} + R \dot{q} + \left(\frac{1}{C}\right)q = V_0 \cos \omega t$$

Analogy

mech

x

v

m

b

k

$$\omega_0 = \sqrt{\frac{k}{m}}$$

$$\gamma = \frac{b}{m}$$

electrical

q

I

L

R

$1/C$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\gamma = \frac{R}{L}$$

$$Q = \frac{\omega_0}{\gamma}$$

complexify: $L \ddot{q} + R \dot{q} + \frac{1}{C}q = V_0 e^{i\omega t}$

Impedance Z is the response of the current to an AC voltage


$$I = \frac{V_0 e^{i\omega t}}{Z}$$

[then take real part]

← this eqn defines Z

$|Z|$ describes the "resistance" and the phase of Z describes how much the current leads or lags the driving voltage

① resistor

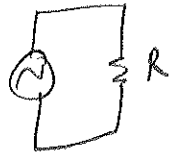


$$V_R = IR = V_0 e^{i\omega t}$$

$$I = \frac{V_0 e^{i\omega t}}{R}$$

$$\Rightarrow Z_R = R$$

② inductor

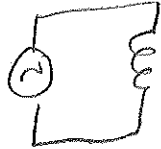

$$V = L \frac{dI}{dt} = V_0 e^{i\omega t}$$

$$\frac{dI}{dt} = \frac{V_0}{L} e^{i\omega t}$$

$$I = \frac{V_0}{i\omega L} e^{i\omega t} \Rightarrow Z_L = i\omega L$$

$$= \frac{V_0}{\omega L} e^{i(\omega t - \frac{\pi}{2})}$$

↑ current lags voltage by 90°

③ capacitor



$$V_c = q/C = V_0 e^{i\omega t}$$

$$q = CV_0 e^{i\omega t}$$

$$I = \omega C V_0 e^{i\omega t} = \frac{V_0 e^{i\omega t}}{(\frac{1}{\omega C})}$$

$$\Rightarrow Z_C = \frac{1}{i\omega C}$$

$$= \omega C V_0 e^{i(\omega t + \frac{\pi}{2})}$$

↑ current leads voltage by 90°

Impedances of elements in series add $Z = Z_1 + Z_2$

" " " " parallel add in reverse, $\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2}$

RLC circuit: $Z = Z_R + Z_L + Z_C = R + i\omega L - \frac{i}{\omega C}$

Mechanical impedance Z characterizes the response of the (steady state) velocity to a harmonic driving force

$$\dot{x} = \frac{F_0 e^{i\omega t}}{Z}$$

Recall $m\ddot{x} + b\dot{x} + kx = F_0 e^{i\omega t}$

steady state solution $x = C e^{i\omega t}$

$$\Rightarrow C = \frac{F_0}{-m\omega^2 + i b \omega + k}$$

$$\dot{x} = i\omega C e^{i\omega t}$$

$$= \frac{F_0 e^{i\omega t}}{(i m \omega + b - i \frac{k}{\omega})}$$

$$\Rightarrow Z = b + i m \omega - \frac{i k}{\omega}$$

electrical
analog $Z = R + i\omega L + \frac{1}{i\omega C}$
R, L, C in series

$$= b \left[1 + i \left(\frac{m}{b} \omega - \frac{k}{b\omega} \right) \right]$$

$$= b \left[1 + i Q \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \right] \quad \text{Recall } \begin{cases} \omega_0 = \sqrt{\frac{k}{m}} \\ Q = \frac{\omega_0}{\gamma} = \frac{\sqrt{k m}}{b} \end{cases}$$

$$|Z| = b \sqrt{1 + Q^2 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^2}, \text{ minimized at } \omega = \omega_0$$

$$\dot{x} = \text{Re} \left[\frac{F_0}{z} e^{i\omega t} \right]$$

$$= \text{Re} \left[\frac{F_0}{|z|} e^{i(\omega t + \phi + \frac{\pi}{2})} \right]$$

$$= \frac{F_0}{|z|} \cos(\omega t + \phi + \frac{\pi}{2})$$

velocity leads displacement by $\frac{\pi}{2}$ since $\dot{x} = i\omega C e^{i\omega t}$

Amplitude of velocity = $\frac{F_0}{|z|}$, maximized at $\omega = \omega_0$


Power dissipated by a damped driven oscillator (steady state)

work done by damping force $dW = \vec{F}_{\text{damp}} \cdot d\vec{r}$

$$\text{power dissipated } P = \frac{dW}{dt} = \vec{F}_{\text{damp}} \cdot \frac{d\vec{r}}{dt} = (-b\dot{x}) \cdot \dot{x} = -b\dot{x}^2$$

$$P = -b \frac{F_0^2}{|z|^2} \cos^2(\omega t + \phi + \frac{\pi}{2})$$

$$\langle P_{\text{damp}} \rangle = -\frac{bF_0^2}{2|z|^2}$$

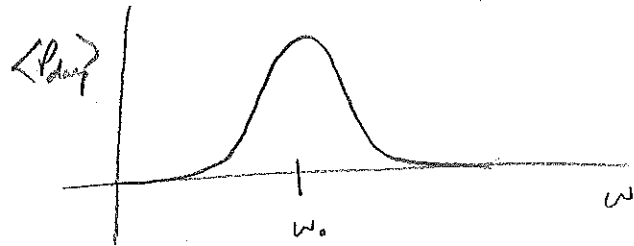


max power dissipated at $\omega = \omega_0$ where $|z| = b \Rightarrow \langle P_{\text{damp}} \rangle = -\frac{F_0^2}{2b}$

[seems surprising that this is large for lightly damped
→ due to large velocity at resonance]

NOT FOR CLASS

(J)

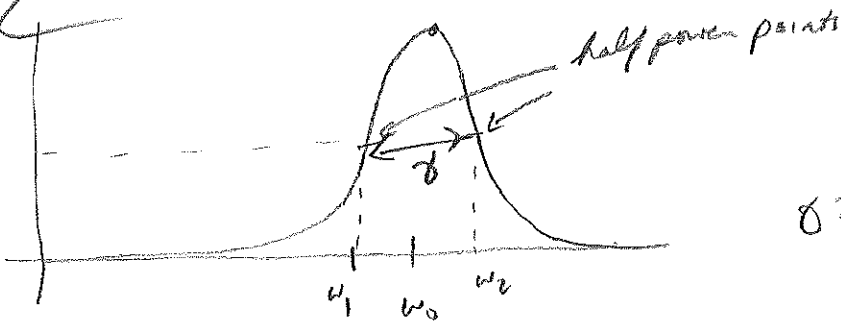

$\delta = \text{width}$
(FWHM)

Similar to
Problem 6
(prob set 5)

$$I = I_0 \left[1 + Q^2 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^2 \right]^{-1}$$

$$\langle I \rangle = \frac{T_0^2}{26 \left[1 + Q^2 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^2 \right]}$$

At half power points $[] = 2$

$$Q^2 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^2 = 1$$

$$\frac{\omega^2 - \omega_0^2}{\omega \omega_0} = \pm \frac{1}{Q}$$

$$\omega^2 \mp \frac{\omega_0}{Q} \omega - \omega_0^2 = 0$$

$$\frac{(\omega - \omega_0)(\omega + \omega_0)}{\omega \omega_0} = \pm \frac{1}{Q}$$

$$\omega^2 \mp \frac{\omega_0}{Q} \omega - \omega_0^2 = 0$$

$$\omega = \frac{1}{2} \left[\pm \frac{\omega_0}{Q} + \sqrt{\frac{\omega_0^2}{Q^2} + 4\omega_0^2} \right]$$

$$\omega_2 > \omega_0 \text{ so}$$

$$\frac{(\omega_2 - \omega_0)(\omega_2 + \omega_0)}{\omega_2 \omega_0} = \frac{1}{Q}$$

$$\Delta \omega = \frac{\omega_0}{Q} = \delta$$

$$\omega_1 < \omega_0 \text{ so}$$

$$\frac{(\omega_1 - \omega_0)(\omega_1 + \omega_0)}{\omega_1 \omega_0} = -\frac{1}{Q}$$