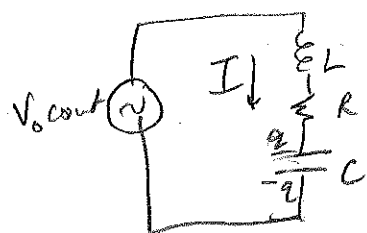


mechanical damped driven oscillator $m\ddot{x} + b\dot{x} + kx = F_0 \cos \omega t$

[They've seen RLC circuits in the problem]

RLC circuit w/ AC driving voltage



Let q = charge on capacitor (upper plate)

$$I = \frac{dq}{dt}$$

$$V_L + V_R + V_C = V_0 \cos \omega t$$

$$L \frac{dI}{dt} + RI + \frac{q}{C} = V_0 \cos \omega t$$

$$L \dot{q} + R \dot{q} + \left(\frac{1}{C}\right)q = V_0 \cos \omega t$$

Analogy

mech

x

v

m

b

k

$$\omega_0 = \sqrt{\frac{k}{m}}$$

$$\gamma = \frac{b}{m}$$

$$Q = \frac{\omega_0}{\gamma}$$

electrical

q

I

L

R

$1/C$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\gamma = \frac{R}{L}$$

complexity: $L\ddot{q} + R\dot{q} + \frac{1}{C}q = V_0 e^{i\omega t}$


Impedance Z is the response of the current to an AC voltage

$$I = \frac{V_0 e^{i\omega t}}{Z} \quad \left[\text{then take real part} \right]$$

← this eqn defines Z

$|Z|$ describes the "resistance" and the phase of Z describes how much the current leads or lags the driving voltage


① Resistor

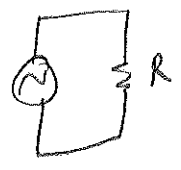

$$V_R = IR = V_0 e^{i\omega t}$$

$$I = \frac{V_0 e^{i\omega t}}{R} \Rightarrow Z_R = R$$

② Inductor

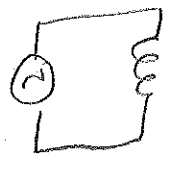

$$V_L = L \frac{dI}{dt} = V_0 e^{i\omega t}$$


$$\frac{dI}{dt} = \frac{V_0}{L} e^{i\omega t}$$

$$I = \frac{V_0}{i\omega L} e^{i\omega t} \Rightarrow Z_L = i\omega L$$

$$= \frac{V_0}{\omega L} e^{i(\omega t - \frac{\pi}{2})}$$

↑ current lags voltage by 90°

③ Capacitor

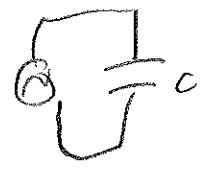

$$V_C = q/C = V_0 e^{i\omega t}$$

$$q = CV_0 e^{i\omega t}$$

$$I = \omega C V_0 e^{i\omega t} = \frac{V_0 e^{i\omega t}}{(\frac{1}{i\omega C})} \Rightarrow Z_C = \frac{1}{i\omega C}$$

$$= \omega C V_0 e^{i(\omega t + \frac{\pi}{2})}$$

↑ current leads voltage by 90°

Impedances of elements in series add $Z = Z_1 + Z_2$

" " " " parallel add in series $\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2}$

RLC circuit: $Z = Z_R + Z_L + Z_C = R + i\omega L - \frac{i}{\omega C}$

Mechanical impedance Z characterizes the response of the steady state velocity to a harmonic driving force

$$\dot{x} = \frac{F_0 e^{i\omega t}}{Z}$$

[N.B. don't include A here]

Recall $m\ddot{x} + b\dot{x} + kx = F_0 e^{i\omega t}$

$$x = C e^{i\omega t} \quad (\text{steady state})$$

$$\Rightarrow C = \frac{F_0}{-m\omega^2 + ib\omega + k} = A e^{i\phi} \quad \text{where} \quad \begin{cases} A = \frac{F_0/m}{\sqrt{(\omega^2 - \omega_0^2)^2 + (\gamma\omega)^2}} \\ \phi = -\arctan\left(\frac{\gamma\omega}{\omega_0^2 - \omega^2}\right) \end{cases}$$

$$\dot{x} = i\omega C e^{i\omega t} = e^{i\frac{\pi}{2}} \omega (A e^{i\phi}) e^{i\omega t} = \omega A e^{i(\omega t + \phi + \frac{\pi}{2})}$$

hold onto this for a moment

$$\dot{x} = \frac{F_0}{(im\omega + b - i\frac{k}{\omega})} e^{i\omega t}$$


$$\Rightarrow Z = b + im\omega - i\frac{k}{\omega} \quad (\text{check analogy of electrical})$$

$$= b \left[1 + iQ \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \right]$$

Let $z = |z|e^{-i\phi_v}$

$$|z| = b \sqrt{1 + Q^2 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^2}$$

Minimized at $\omega = \omega_0$

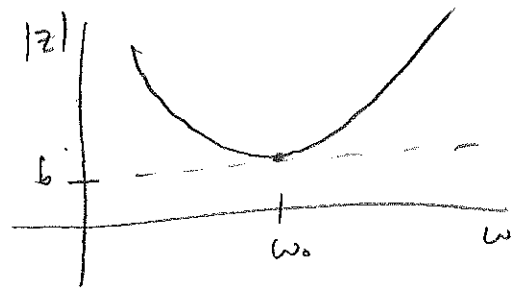


$$\phi_v = -\arctan \left[Q \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \right]$$

The


$$\dot{x} = \frac{F_0}{z} e^{i\omega t} = \frac{F_0}{|z|} e^{i(\omega t + \phi_v)}$$

$$\phi_v = \phi + \frac{\pi}{2}$$
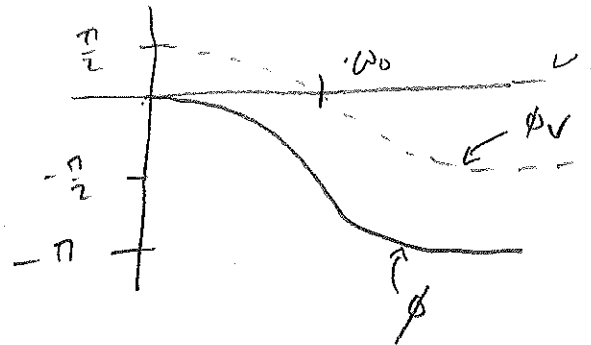
$$\phi_v = 0 \text{ at } \omega = \omega_0$$



amplitude of velocity $= \omega A = \frac{F_0}{|z|}$

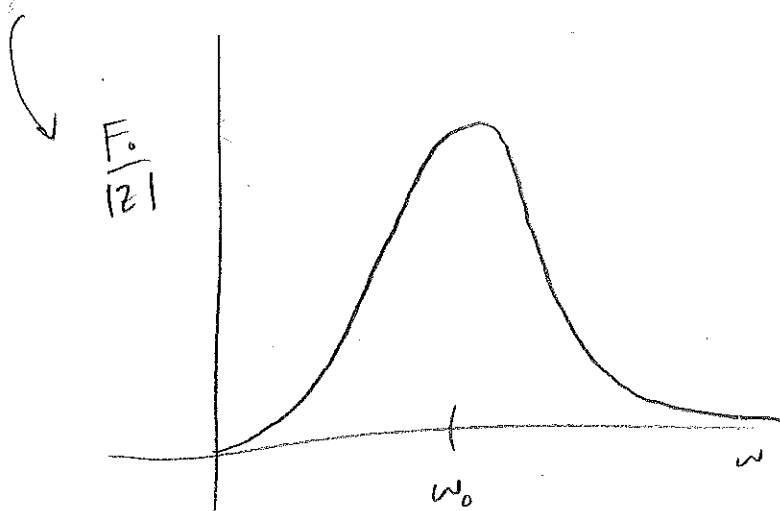

Power dissipated by a damped driven oscillator (Steady state)


work done by friction $dW = \vec{F}_{\text{fric}} \cdot d\vec{r}$

Power dissipated by friction $P = \frac{dW}{dt} = \vec{F}_{\text{fric}} \cdot \vec{v} = (-b\dot{x})\dot{x} = -b\dot{x}^2$

Steady state $\dot{x} = \frac{F_0}{|Z|} \cos(\omega t + \phi_v)$

$$P_{\text{fric}} = -b \frac{F_0^2}{|Z|^2} \cos^2(\omega t + \phi_v)$$

$$\langle P_{\text{fric}} \rangle = -\frac{b}{2} \frac{F_0^2}{|Z|^2}$$

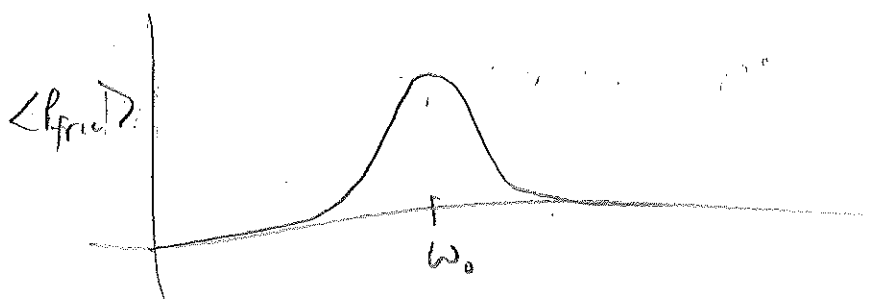

max power dissipated at $\omega = \omega_0$, where $|Z| = b$

$$\Rightarrow \langle P_{\text{fric}} \rangle_{\text{max}} = -\frac{F_0^2}{2b}$$

[the lighter the damping, the more power dissipated]

Driven RLC circuit: $\langle P_{\text{fric}} \rangle = -\frac{R V_0^2}{2|Z|^2}$

$$\langle P_{\text{fric}} \rangle_{\text{max}} = -\frac{V_0^2}{2R}$$